
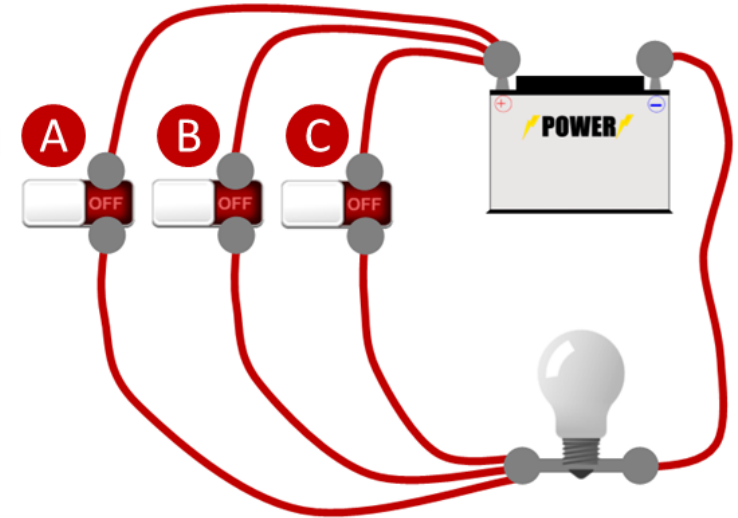
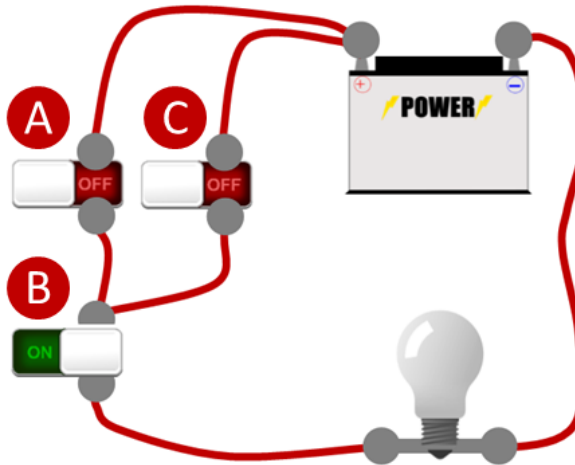


Combinational Logic

Construct the circuits

Complete the truth tables

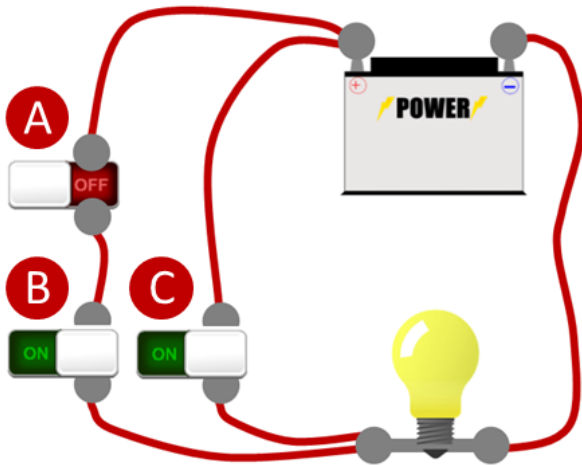

A	B	C	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

[illegible][illegible]